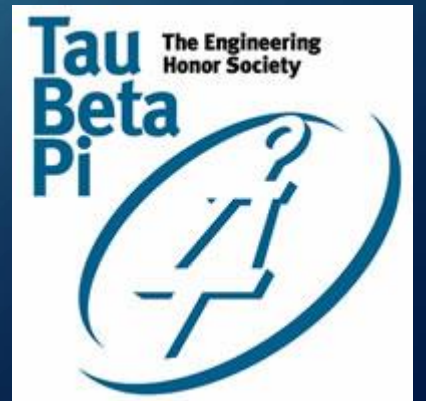


DIGITAL LOGIC



PRESENTATION BY: MATTHEW MORAGUEZ, MATTHEW HARWOOD, AADIL VORA,
RUBEN JEAN

FEBRUARY 18, 2015




WHAT IS DIGITAL LOGIC?

- **Digital logic** forms the foundation for computers. It allows circuits to perform logical operations.
- **Logic gates** are the building blocks used in digital logic. They make simple yes/no decisions.
- By stringing logic gates together, a computer can be made to perform complex tasks.
- In digital logic, we work with two cases:
 - Yes or No, True or False, 1 or 0
- In this class:
 - Output (LED): On is 1, Off is 0
 - Input (Switch): Closed is 1, Open is 0

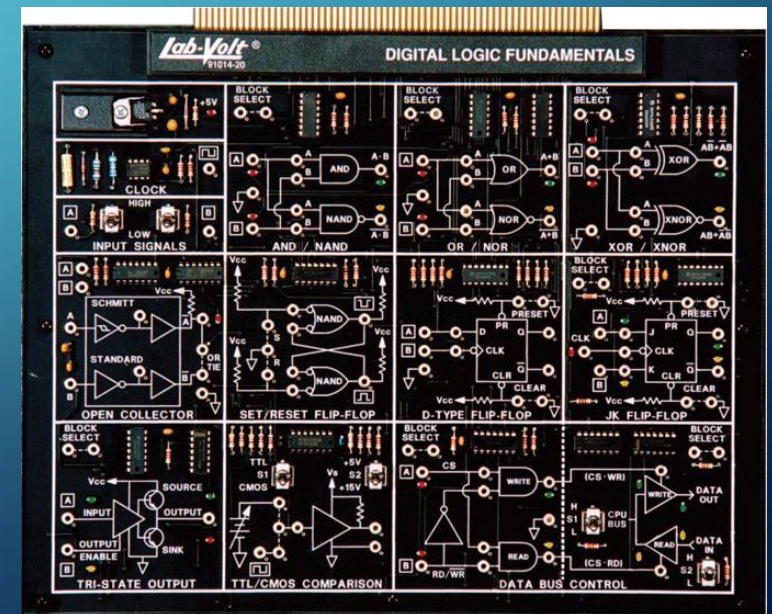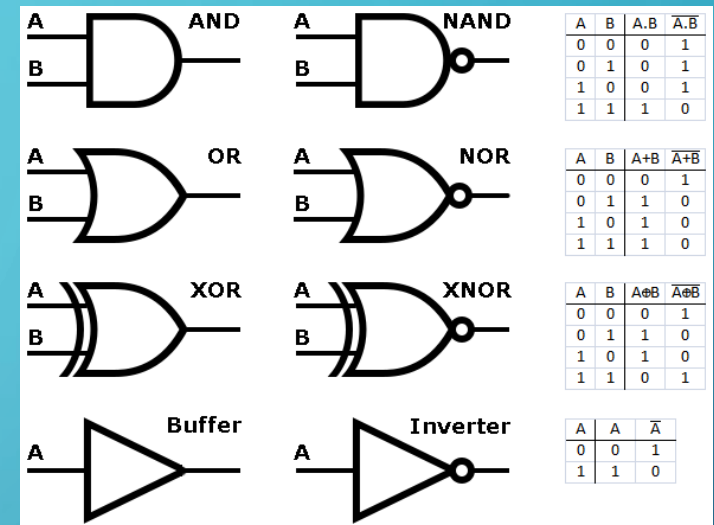

WHAT DO WE DO AS AN ENGINEER?

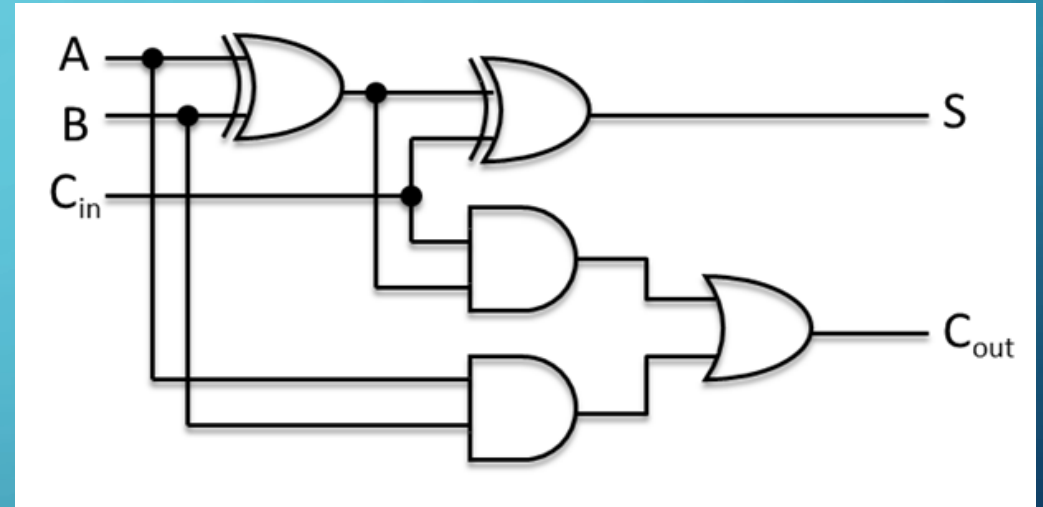- Create digital logic circuits that achieve a desired task.
- Analyze our digital logic circuits to determine their output.



A one-bit fullbinary adder. This circuit adds two numbers A and B and returns the sum S.

LOGIC GATES

The logic gates we will cover today are:

AND (returns true if both inputs are true)

OR (returns true if at least one of the inputs is true)

NOT (returns the opposite of the input)

NOR (returns true if both inputs are false)

NAND (returns false if both inputs are true)

These logic gates form the building blocks of digital logic and can be strung together to make complex circuits.

The inner workings of logic gates typically consist of **transistors**, which are little electrical switches. To make it easier to visualize, we will use mechanical switches in our circuits.

TRUTH TABLES

A **truth table** presents the output of a logical operator for every combination of the input values.


We will use truth tables to explain what each of the logic gates do.

In this class, we will specify a truth table and give you a chance to engineer the circuit to act like we want it to.

We will arrange the two switches and the LED so that the switches open or short the circuit to achieve the desired truth table.


AND GATE

2-input AND gate

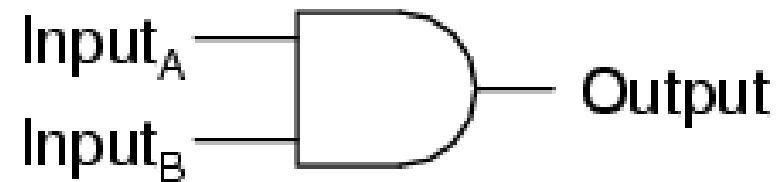


A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1

AND GATE CIRCUIT

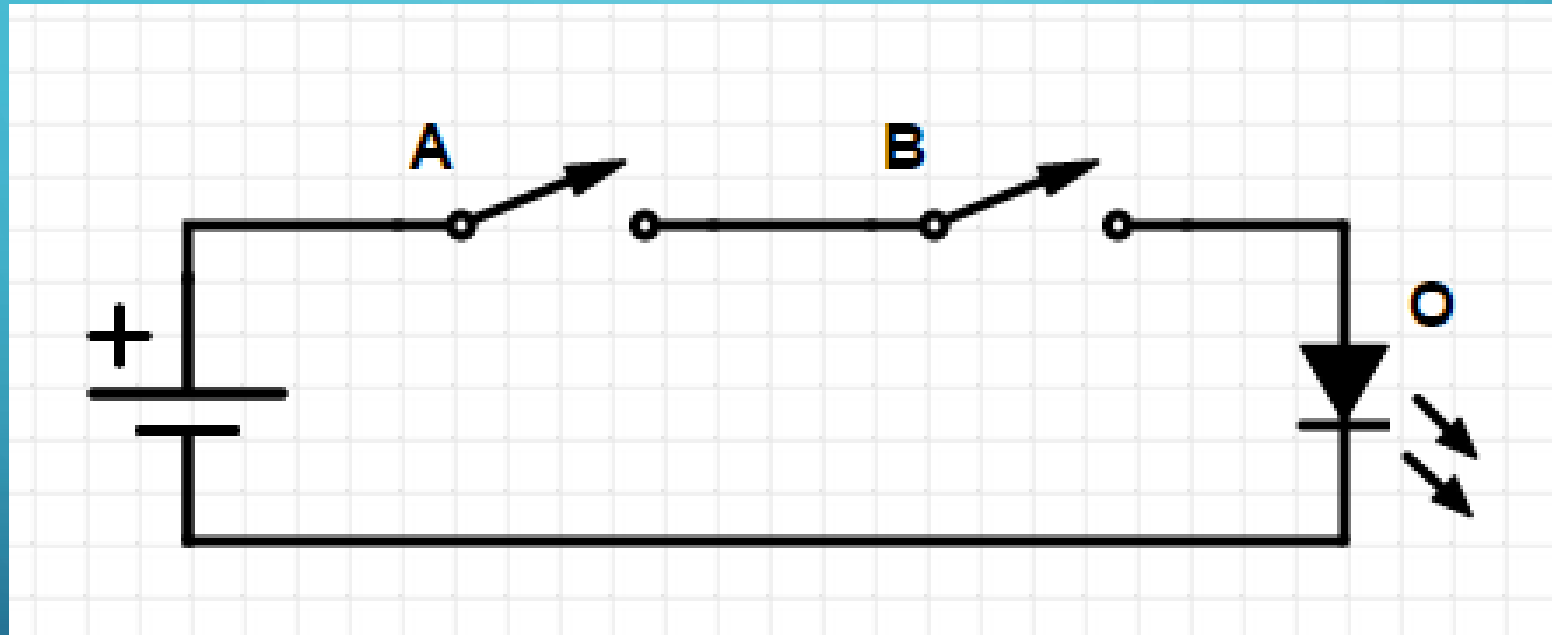


OR GATE

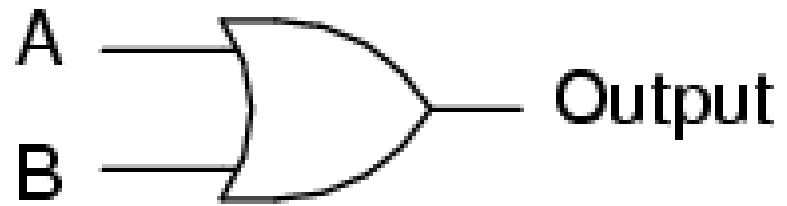


A	B	Output
0	0	0
0	1	1
1	0	1
1	1	1

OR GATE CIRCUIT

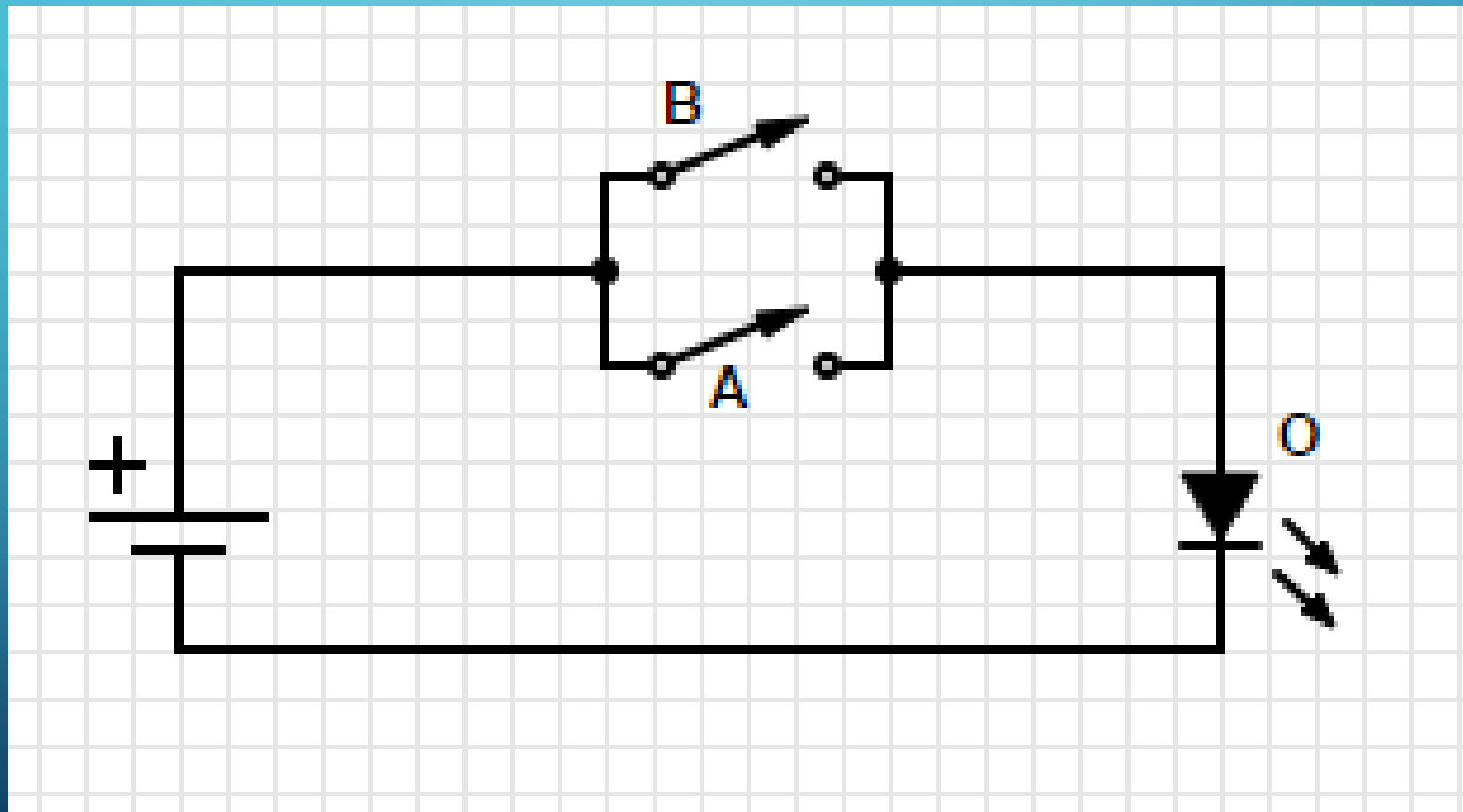


NOT GATE (INVERTER)

INVERTER

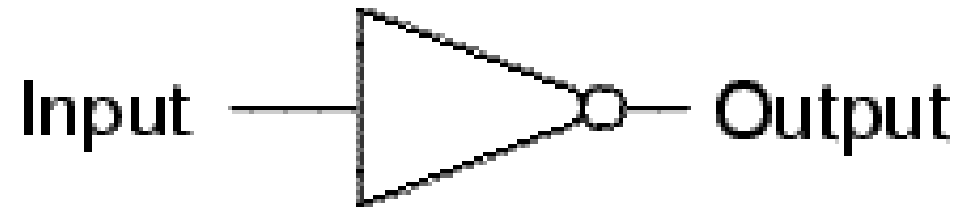


Input	Output
1	0
0	1

NOT GATE CIRCUIT

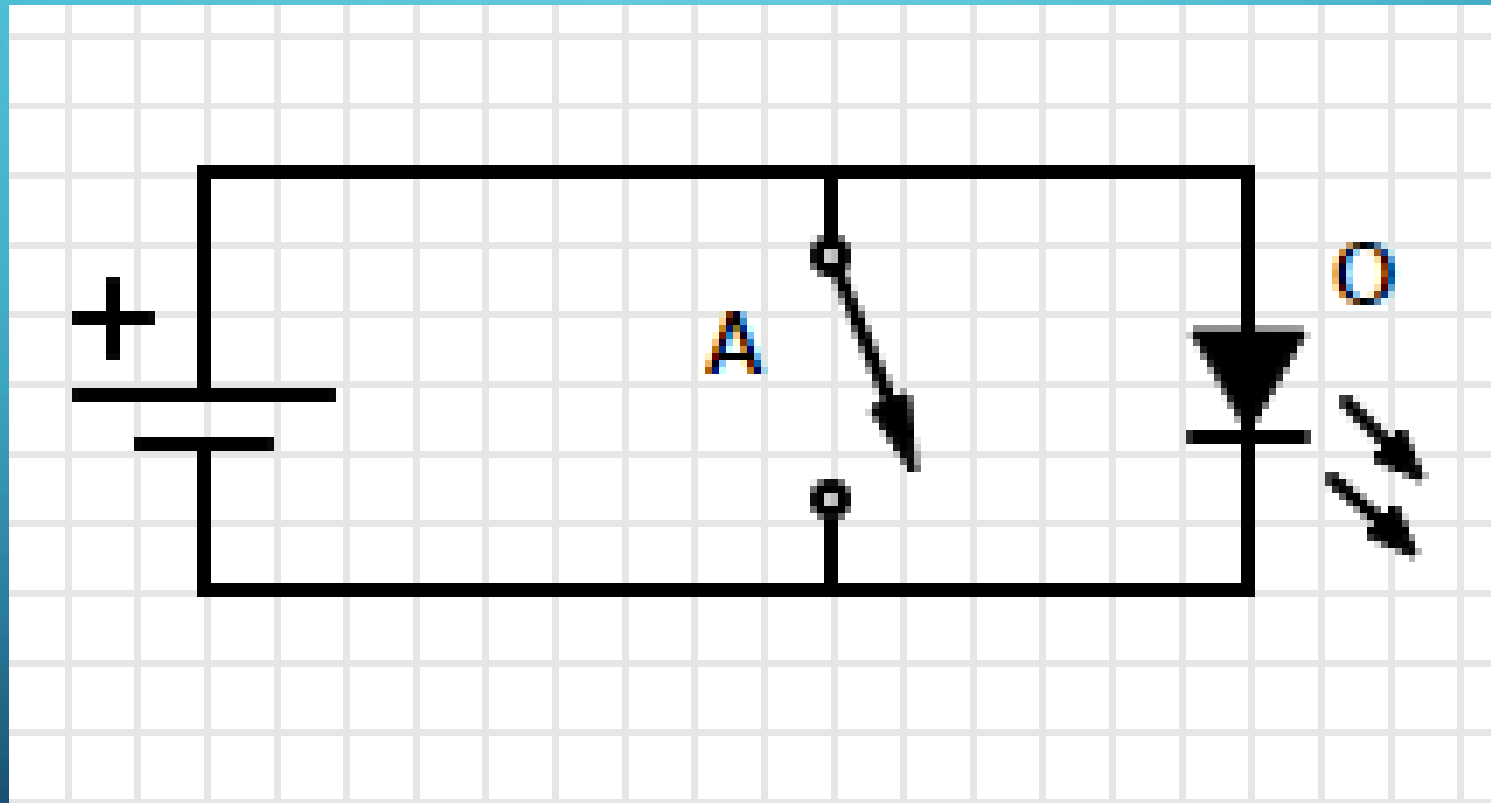


NOR GATE

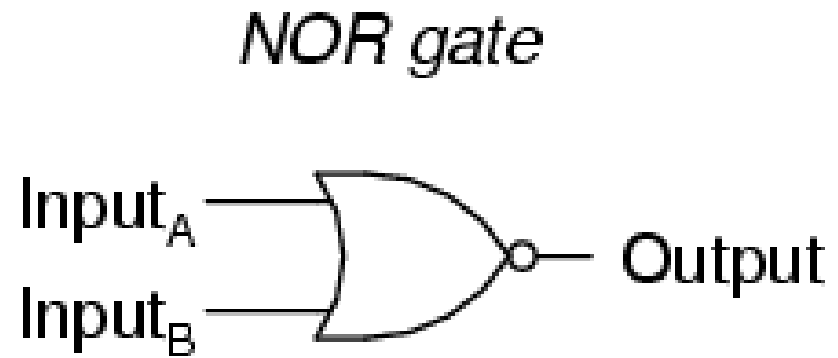


A	B	Output
0	0	1
0	1	0
1	0	0
1	1	0

NOR GATE CIRCUIT

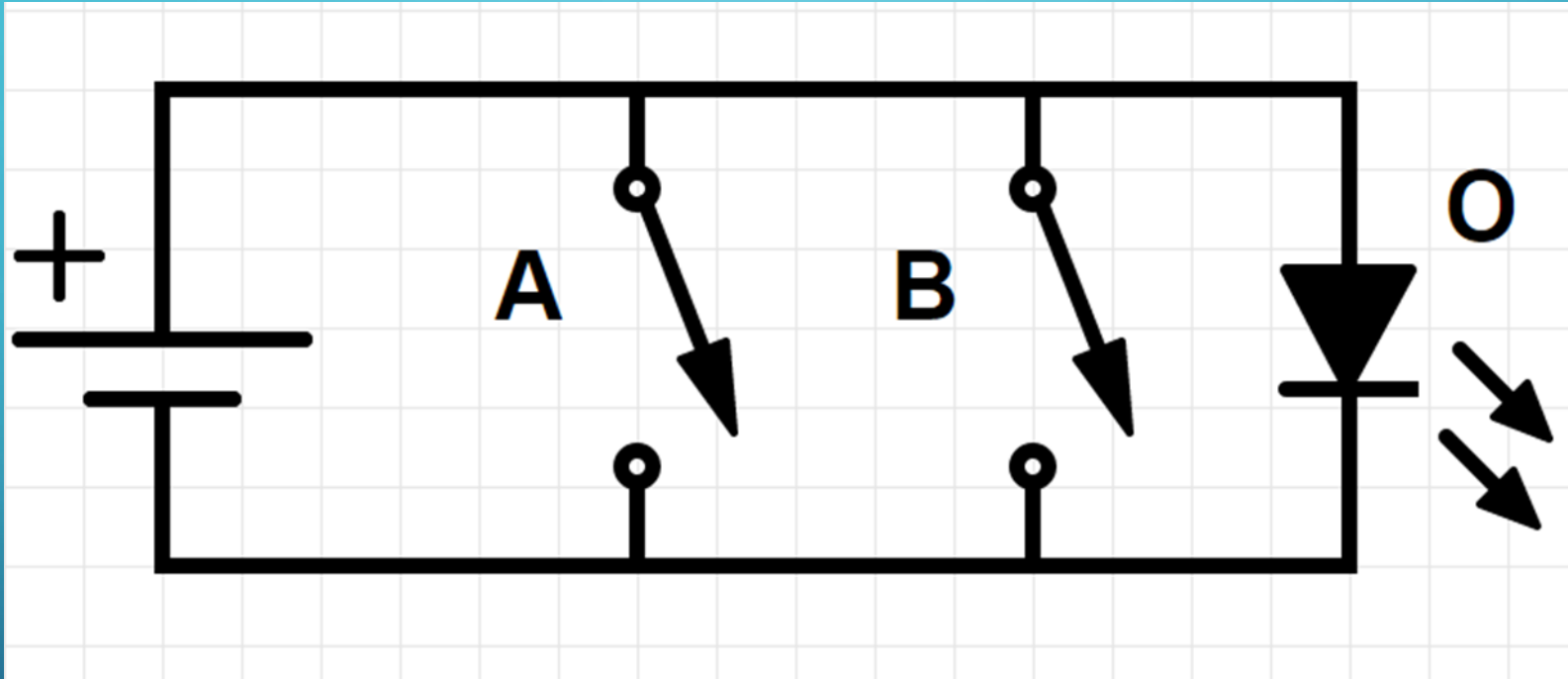


NAND GATE

NAND gate

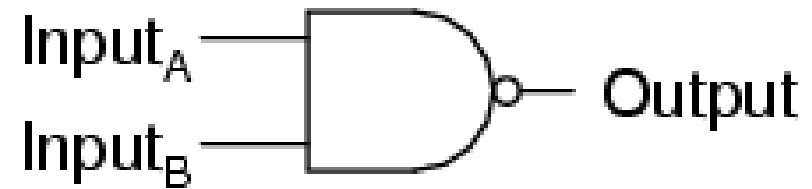

A	B	Output
0	0	1
0	1	1
1	0	1
1	1	0

NAND GATE CIRCUIT

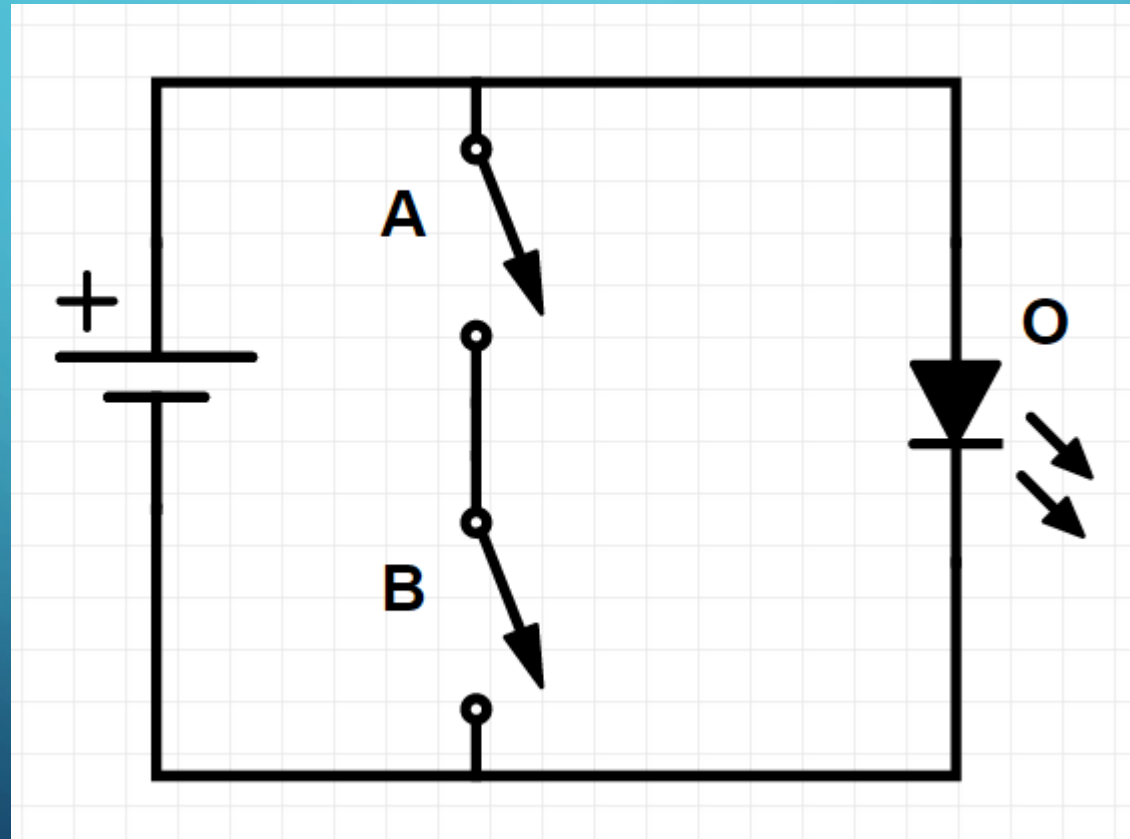

The background is a blue gradient with decorative white circuit-like lines in the corners. The lines consist of straight segments and small circles, resembling a stylized PCB or network diagram.

THANK YOU!