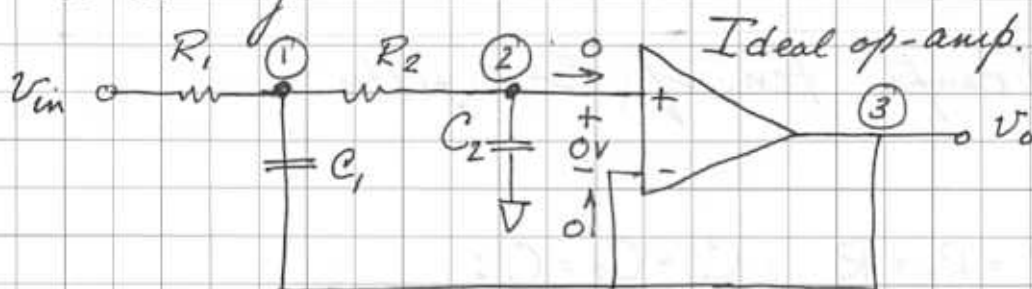


LAB 3: FREQUENCY RESPONSE OF SYSTEMS & DISTORTION

PRELAB

Sallen-Key



$$\textcircled{1} \quad \frac{V_1 - V_{in}}{R_1} + \frac{V_1 - V_2}{R_2} + \frac{V_1 - V_{out}}{1/C_1 s} = 0$$

$$\textcircled{2} \quad \frac{V_2 - V_1}{R_2} + \frac{V_2}{1/C_2 s} = 0$$

$$\textcircled{3} \quad V_2 = V_{out}$$

$$\begin{aligned} \text{Eq. } \textcircled{2} &\Rightarrow -\frac{1}{R_2} V_1 + \left(\frac{1}{R_2} + C_2 s\right) V_{out} = 0 \\ &\Rightarrow (1 + R_2 C_2 s) V_{out} = V_1 \end{aligned}$$

$$\begin{aligned} \text{Eq. } \textcircled{1} &\Rightarrow (R_2 + R_1 + R_1 R_2 C_1 s) V_1 - (R_1 + R_1 R_2 C_1 s) V_{out} = R_2 V_{in} \\ &\Rightarrow (R_1 + R_2 + R_1 R_2 C_1 s) (1 + R_2 C_2 s) V_{out} - (R_1 + R_1 R_2 C_1 s) V_{out} = R_2 V_{in} \end{aligned}$$

$$\begin{aligned} \Rightarrow & \left[\cancel{R_1} + R_2 + \cancel{R_1 R_2 C_1 s} + R_1 R_2 C_2 s + R_2^2 C_2 s + R_1 R_2^2 C_1 C_2 s^2 \right. \\ & \left. - \cancel{R_1} - \cancel{R_1 R_2 C_1 s} \right] V_{out} = R_2 V_{in} \end{aligned}$$

$$\Rightarrow \left[R_2 + (R_1 R_2 C_2 + R_2^2 C_2) s + R_1 R_2^2 C_1 C_2 s^2 \right] V_{out} = R_2 V_{in}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{1}{R_1 R_2 C_1 C_2 s^2 + (R_1 + R_2) C_2 s + 1}$$

Transfer fcn. of S-K filter.

Put $R_1 = R_2 = R$, $C_1 = C_2 = C$:

$$H(s) = \frac{1}{(RC)^2 s^2 + 2RCs + 1}$$

$$\text{also} = \frac{\omega_n^2}{s^2 + 2s\omega_n + \omega_n^2}$$

$$\omega_n^2 = \frac{1}{(RC)^2}, \quad 2s\omega_n = \frac{2}{RC} \Rightarrow \zeta = 1$$

Always critically damped

$$H(\omega) = \frac{1}{1 - (RC)^2 \omega^2 + j2RC\omega}$$

$$|H(\omega)| = \frac{1}{\sqrt{[1 - (RC)^2 \omega^2]^2 + (2RC)^2 \omega^2}}$$

$$H(0) = 1 \quad (= 0 \text{ dB}).$$

$$6 \text{ dB break: } |H(\omega_b)| = \frac{1}{2}$$

$$\Rightarrow \frac{1}{2} = \frac{1}{\sqrt{[1 - (RC)^2 \omega_b^2]^2 + (2RC)^2 \omega_b^2}}$$

$$\Rightarrow [1 - (RC)^2 \omega_b^2]^2 + (2RC)^2 \omega_b^2 - 4 = 0$$

$$\Rightarrow \cancel{(RC)^4 \omega_b^4} + \cancel{(2RC)^2 \omega_b^2} - 3 = 0$$

$$\Rightarrow (RC)^4 \omega_b^4 + 2(RC)^2 \omega_b^2 - 3 = 0$$

$$\Rightarrow \omega_b^2 = \frac{-2(RC)^2 \pm \sqrt{4(RC)^4 + 12(RC)^4}}{2(RC)^4} = \frac{-3}{(RC)^2} \pm \frac{1}{(RC)^2}$$

$$\omega_b^2 = \frac{1}{(RC)^2} \Rightarrow \omega_b = \frac{1}{RC}$$


$$f_b = \frac{1}{2\pi RC}$$

For $R = 8.2 \text{ k}$, $C = 0.01 \mu\text{F}$

$$\omega_b = 12.20 \text{ k rad/s} \quad f_b = \underline{\underline{1.94 \text{ kHz}}}$$

Also: $\omega_n = \frac{1}{RC} = \omega_b$, ~~at ω_n , actual Bode plot is~~ $\zeta = 1$

Straight line Bode plot:

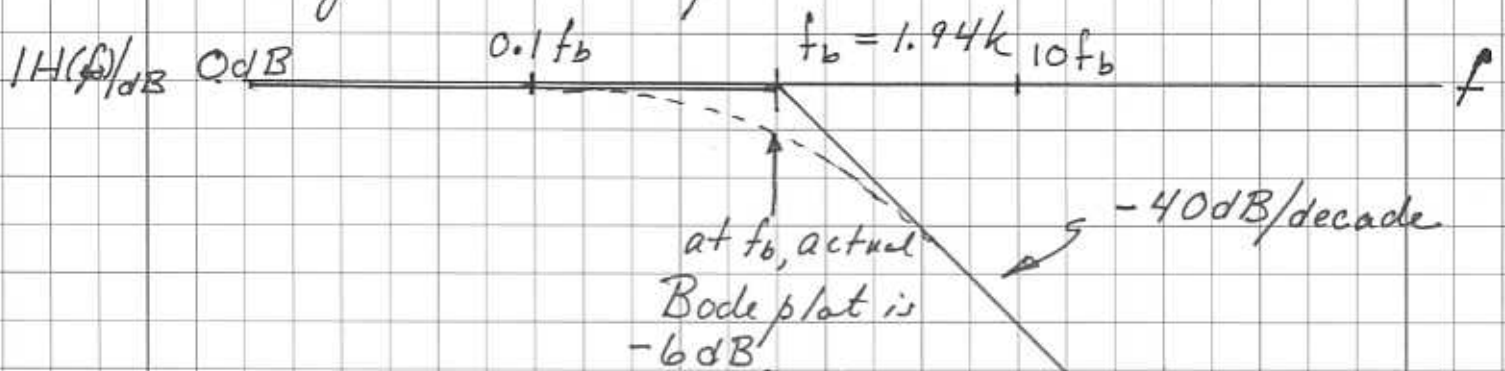

Mathcad,
Bode plots
next two pages

Lab 3 Prelab: Sallen-Key Filter

EEL 4514L: Comm. Laboratory

G. Heitman

Electrical and Computer Engineering

University of Florida

$$R := 8.2 \cdot 10^3 \quad C := 0.01 \cdot 10^{-6}$$

$$f_{\min} := 1 \quad f_{\max} := 10^5 \quad N := 1000 \quad m := 0..N-1$$

$$F_{\min} := \log(f_{\min}) \quad F_{\max} := \log(f_{\max}) \quad F_m := 10^{\left[F_{\min} + m \cdot \frac{(F_{\max} - F_{\min})}{N-1} \right]}$$

These parameters set up a logarithmic sequence of frequencies for the plot.



$$H(s) := \frac{1}{R^2 \cdot C^2 \cdot s^2 + 2 \cdot R \cdot C \cdot s + 1} \quad \text{Sallen-Key transfer function}$$

$$A(f) := 20 \cdot \log(|H(j \cdot 2 \cdot \pi \cdot f)|) \quad \text{Magnitude response}$$

$$\theta(f) := \frac{\arg(H(j \cdot 2 \cdot \pi \cdot f))}{\pi} \quad \text{Phase response, in multiples of } \pi$$

$$f_b := \frac{1}{2 \cdot \pi \cdot R \cdot C} \quad f_b = 1.941 \times 10^3 \quad \text{6dB break frequency} \quad A(f_b) = -6.021$$

$$\theta(f_b) = -0.5$$

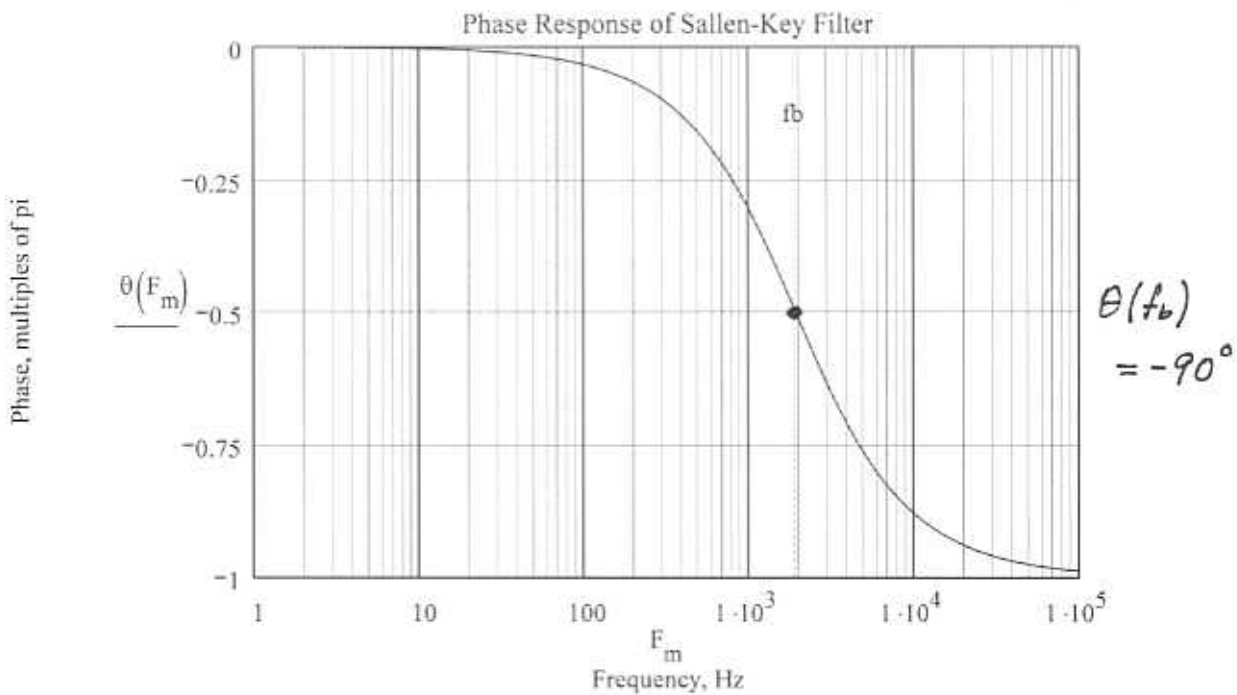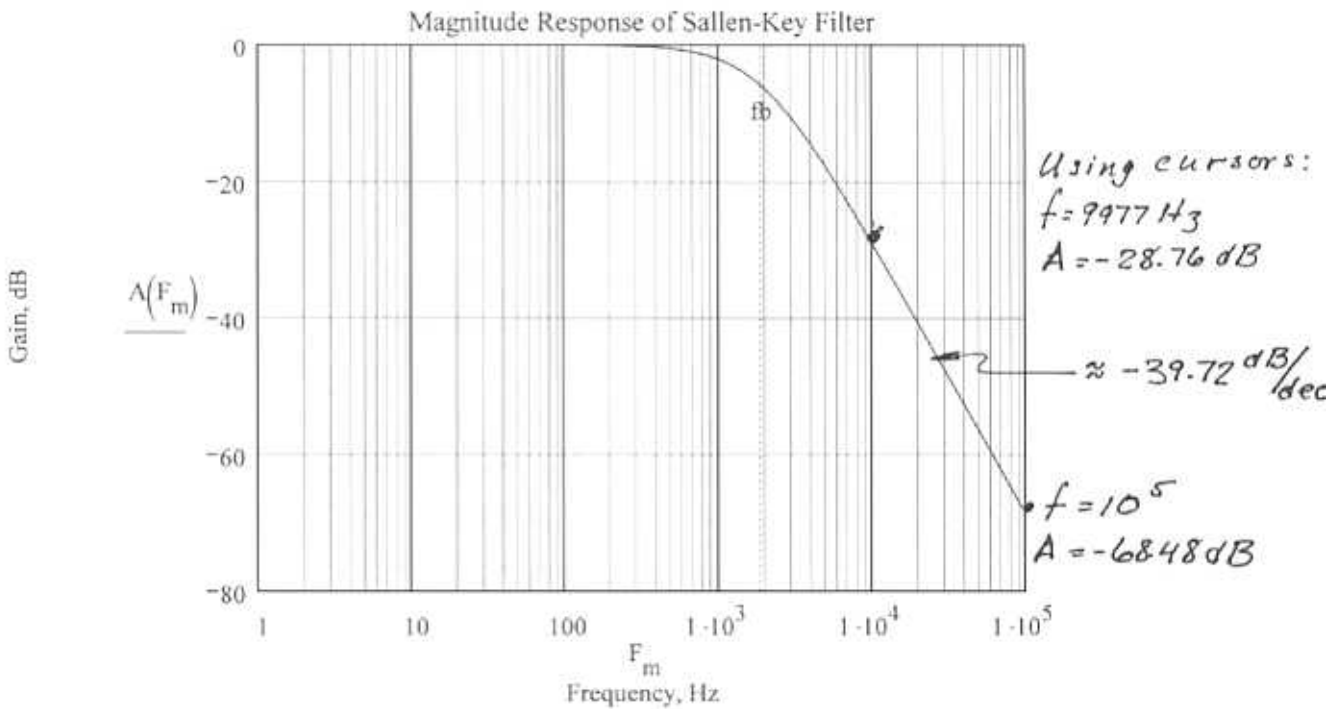


*PSpice simulations—
following pages*

1

2

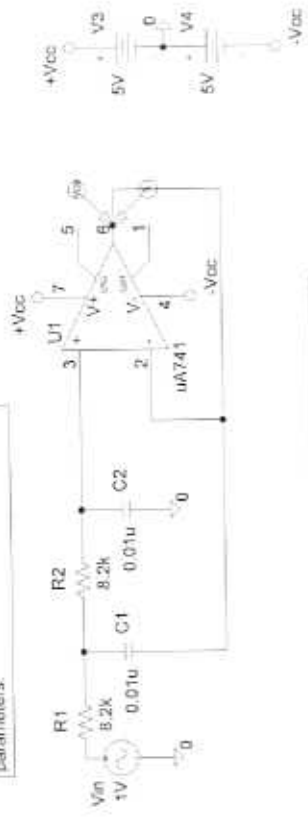Setup for frequency response of Sallen-Key circuit. Vin is a VAC part. In the Analysis Setup, check AC Sweep and enter parameters.



Note: set |Vin|=1V. Then output voltage amplitude is equal to gain.

B


A

B

A

1


2

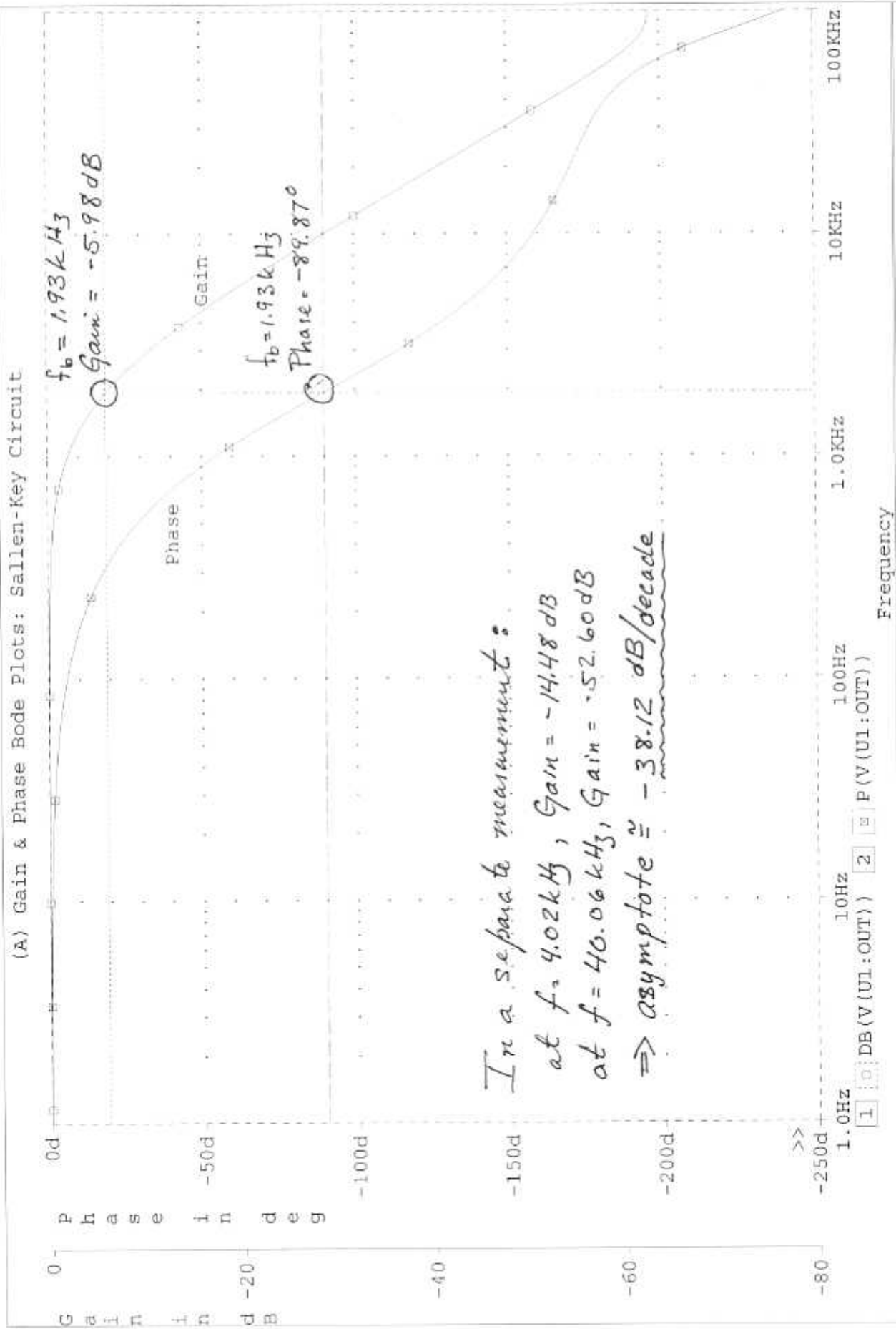

1

2

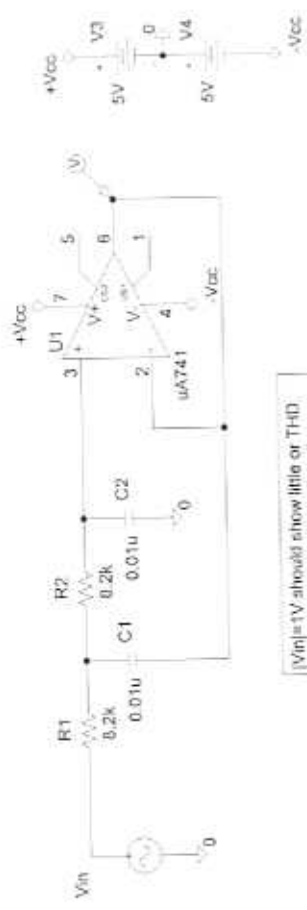Measuring distortion in the Sallen-Key filter. For THD, V_{in} is a sinusoid (in this case 500Hz). Plot V_{out} and then use the FFT in Probe to view the spectrum of V_{out} .



$|V_{in}|=1V$ should show little or THD
 $|V_{in}|=0V$ should show distortion.

B

A

B


A

1

2

* C:\MyDocuments\Courses\Comm\4514Lab\LabMan02\PreLabs\PreLab3_Sa1Kdist.sch
Temperature: 27.0

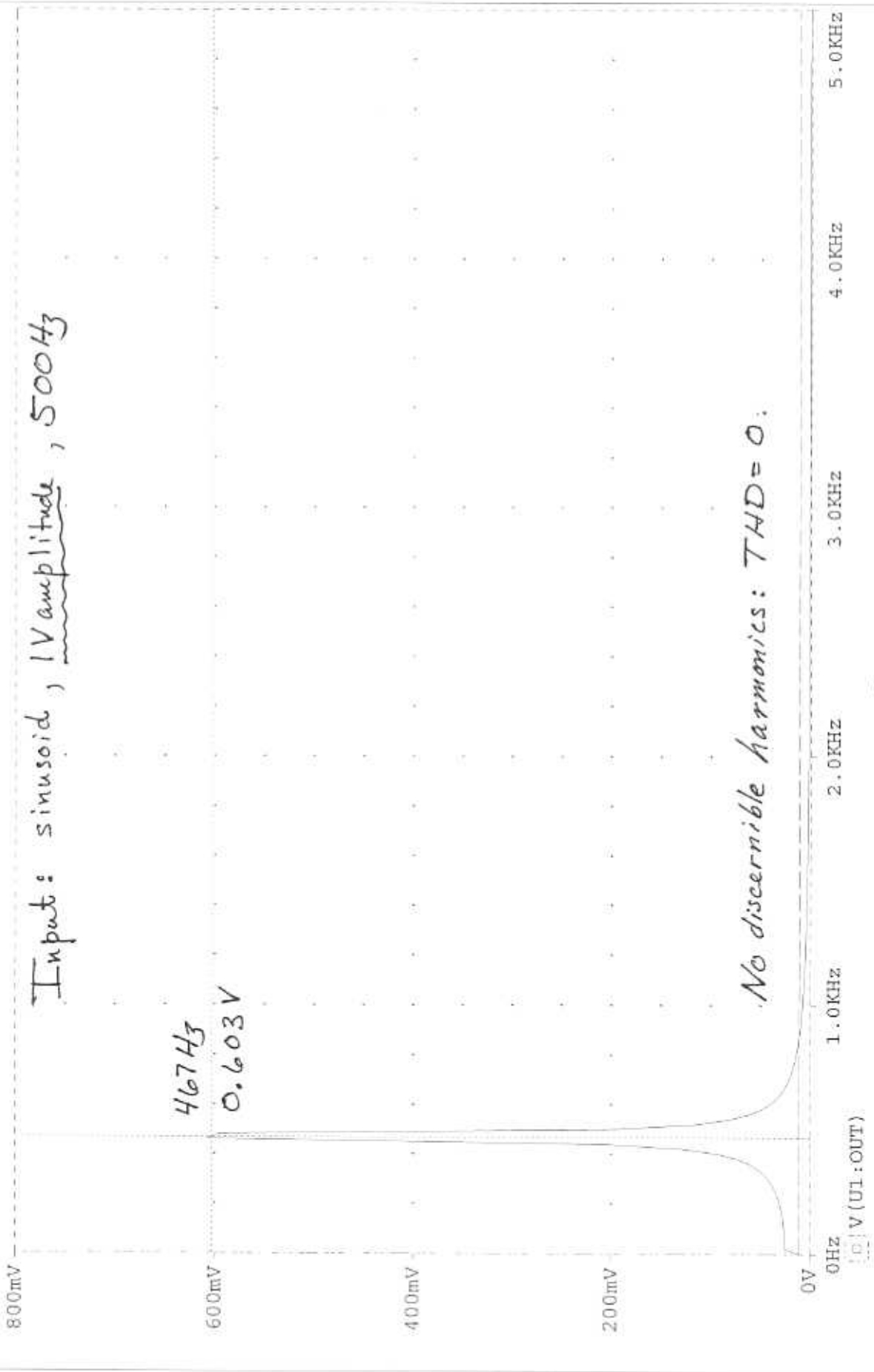(B) Sallen-Key Circuit Distortion Analysis




B1: (467.000, 603.192m) B2: (0.000, 11.172m) DIFF(B): (467.000, 592.020m)

* C:\MyDocuments\Courses\Comm\4514Lab\LabMan02\PreLabs\PreLab3_salKdist.sch
Temperature: 27.0

(B) Sallen-Key Circuit Distortion Analysis

Input: sinusoid, 6V amplitude, 500Hz

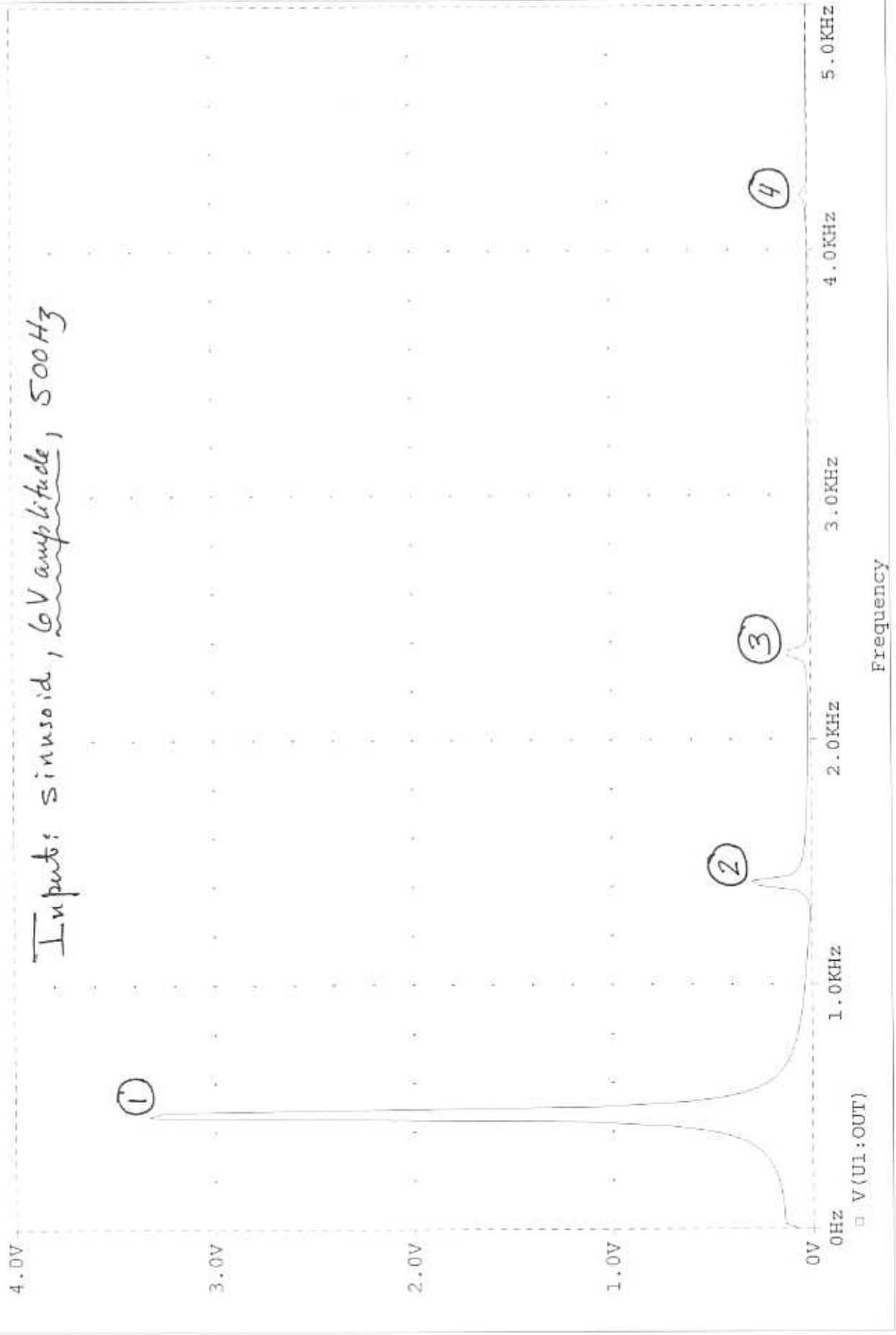

With $|V_{in}| = 1V$, at $500Hz$, there is no discernible distortion. (p45)

With $|V_{in}| = 6V$:

	f, Hz	Line ampl., V	V_n/V_1
①	473.12	3.287 V	—
②	1.42 k	297.9 mV	0.0906
③	2.350 k	115.4 mV	0.0351
④	4.22 k	35.69 mV	0.0108

No lines discernible at higher frequencies.

Use Eq. (4-47) in Couch (also given in lecture):

$$THD = \frac{\sqrt{\sum_{n=2}^{\infty} V_n^2}}{V_1} \times 100\% = \sqrt{\sum_{n=2}^{\infty} \left(\frac{V_n}{V_1}\right)^2} \times 100\%$$

where V_n = amplitude of n^{th} harmonic. From table:

$$\begin{aligned} THD &= \sqrt{(.0906)^2 + (.0351)^2 + (.0108)^2} \times 100\% \\ &= \underline{\underline{9.78\%}} \end{aligned}$$